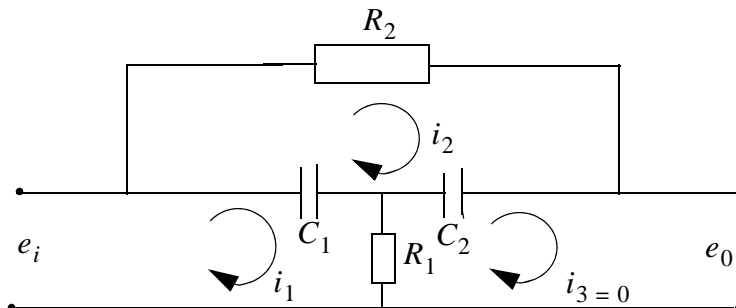


LINEAR SYSTEMS CONTROL

Solutions to Problems

Problem 2.5

a. The first filter (a.) is:




With the mask currents as drawn and using Ohm's law, one obtains:

$$e_i = \frac{1}{C_1} \int (i_1 - i_2) dt + R_1 i_1$$

$$0 = \frac{1}{C_1} \int (i_2 - i_1) dt + R_2 i_2 + \frac{1}{C_2} \int i_2 dt$$

$$-e_0 = -R_1 i_1 - \frac{1}{C_2} \int i_2 dt$$

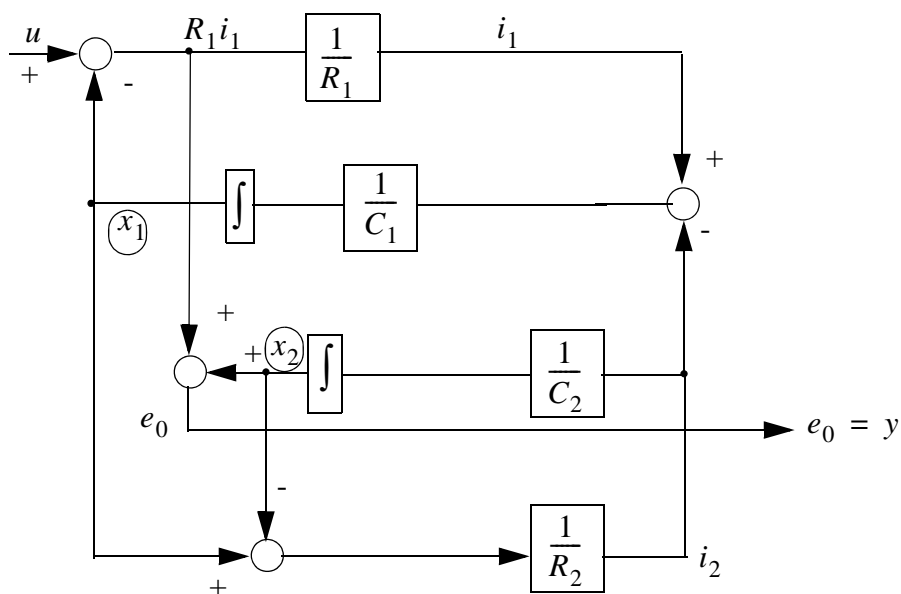b. These equations have the block diagram below:



LINEAR SYSTEMS CONTROL

Solutions to Problems

Problem 2.5 (continued)

c. The state equations for bridged T filter (a.) are:

$$\dot{x}_1 = \frac{1}{C_1} \left(\frac{1}{R_1} (u - x_1) - \frac{1}{R_2} (x_1 - x_2) \right)$$

$$\dot{x}_2 = \frac{1}{C_2} \frac{1}{R_2} (x_1 - x_2)$$

$$y = e_0 = x_2 - x_1 + u$$


$$\dot{x}_1 = \frac{1}{C_1 R_1} u - \frac{1}{C_1 R_1} x_1 - \frac{1}{C_1 R_2} x_1 + \frac{1}{C_1 R_2} x_2$$

$$\dot{x}_2 = \frac{1}{C_2 R_2} x_1 - \frac{1}{C_2 R_2} x_2$$

$$\dot{\mathbf{x}} = \begin{bmatrix} -\frac{R_1 + R_2}{C_1 R_1 R_2} & \frac{1}{C_1 R_2} \\ \frac{1}{C_2 R_2} & -\frac{1}{C_2 R_2} \end{bmatrix} \mathbf{x} + \begin{bmatrix} \frac{1}{C_1 R_1} \\ 0 \end{bmatrix} u$$

$$\mathbf{y} = [-1 \quad 1] \mathbf{x} + u$$

The second filter (b.) is:

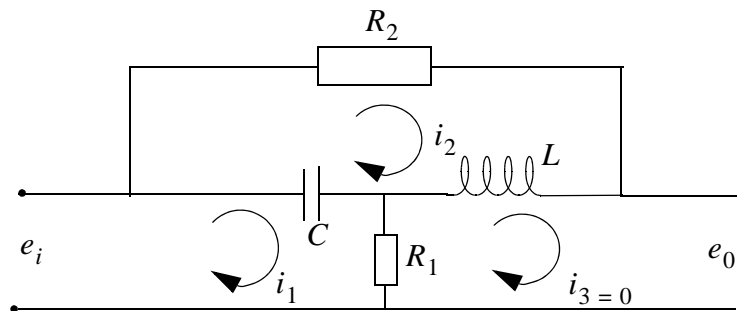

This filter is described by the mesh equations:

LINEAR SYSTEMS CONTROL

Solutions to Problems


Problem 2.5 (continued)

$$e_i = \frac{1}{C} \int (i_1 - i_2) dt + R_1 i_1$$

$$0 = \frac{1}{C} \int (i_2 - i_1) dt + R_2 i_2 + L \frac{di_2}{dt}$$

$$-e_0 = -R_1 i_1 - L \frac{di_2}{dt}$$

With the block diagram:

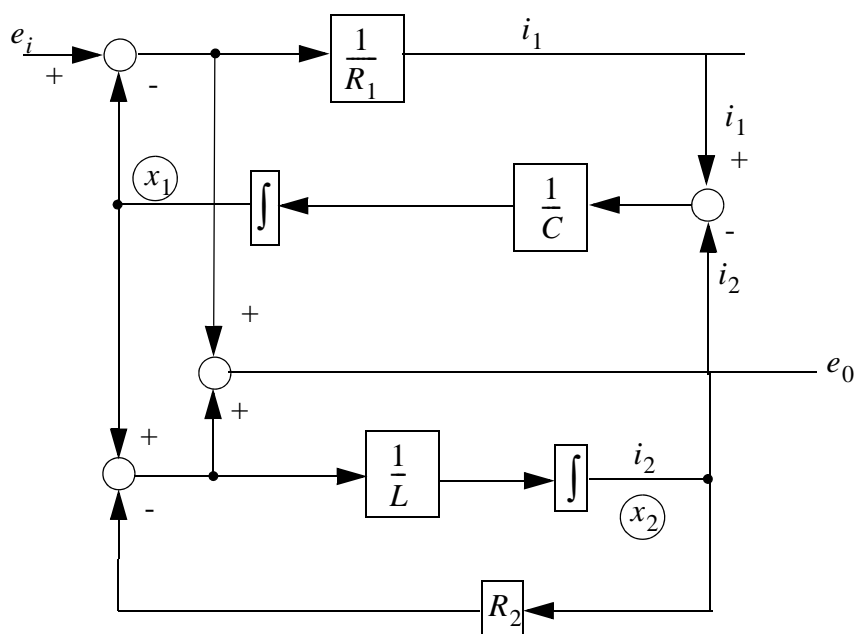

This block diagram can be translated into the state equations:

$$\dot{x}_1 = \frac{1}{C} \left(\frac{1}{R_1} (e_i - x_1) - x_2 \right) = \frac{1}{CR_1} e_i - \frac{1}{CR_1} x_1 - \frac{1}{C} x_2$$

$$\dot{x}_2 = \frac{1}{L}(-R_2x_2 + x_1) = -\frac{R_2}{L}x_2 + \frac{1}{L}x_1$$

$$y = e_i - x_1 + x_1 - R_2 x_2$$

LINEAR SYSTEMS CONTROL**Solutions to Problems**

Problem 2.5 (continued)

$$\dot{\mathbf{x}} = \begin{bmatrix} -\frac{1}{CR_1} & -\frac{1}{C} \\ \frac{1}{L} & -\frac{R_2}{L} \end{bmatrix} \mathbf{x} + \begin{bmatrix} \frac{1}{CR_1} \\ 0 \end{bmatrix} e_i$$

$$\mathbf{y} = [0 \quad -R_2] \mathbf{x} + e_i$$

